

CK1213 - 40 Second Message Recorder with Looping Option

Information Storage Devices are one of the leaders in solid state audio recording & playback devices. The latest ISD25xx series provides high-quality, single-chip, non-volatile record/playback for 40, 60, 75, 90 & 120 seconds. These CMOS devices include an on-chip oscillator, microphone preamplifier, automatic gain control, antialiasing filter, smoothing filter and speaker amplifier. In addition it is micro-processor compatible allowing complex messaging and addressing to be achieved.

Recordings are stored in on-board non-volatile memory cells, providing zero power message storage. The proprietary storage method allows natural voice analog storage. The purpose of this Kit is to introduce you to this modern, new technology.

Our Circuit. We use the ISD2540, 40 second audio recording IC in this kit. The ISD2540 has several modes of operation. We use it here as a multi-message recorder. You may record as many messages as you want up to 40 seconds of memory space. Put the SPDT switch into the Record position and just push & release the Start/Pause button to start recording. The Record LED goes on. Push the Start/Pause button to Pause - stop recording. That is the end of Message 1.

Sometime later you can record a follow on message, Message 2, by pushing the Start/Pause button again. When you put the switch to Play the messages will playback. Only one message will be played back at a time. You must push Start/Pause again to get the next message. The Reset switch will move the internal address pointer back to the start of the memory space.

But we also provide the option to endlessly loop the first message. Move the switch from NORMAL to LOOP. The first message will now be endlessly repeated. So you can record a 40 second message and have it played back continuously. If you attach switches to the pads of the push buttons then the recorder may be activated when people are moving past a certain point.

Removing the power will not destroy the messages. You may, for example, record a long message, then send just the IC to someone through the mail then the friend could playback your message. This is the same as the 20 second Greeting Cards now on the market. They use a ISD1420 chip-on-board IC. Longer recording ISD chips are able to be used in this kit: 60, 90 and 120 second ISD chips may be plugged in.

Build up the Kit and start playing with it. Far better to learn about it from actual use than reading pages about how it works!

You can get more about applications and memory addressing of the ISD25xxx from the ISD website at

<http://www.isd.com>

Go to Products/Voice Record, Playback & Text-to-Speech / Product Data Sheets.

Construction. We have placed some of the components underneath the IC. This was not only to reduce the size of the PCB. Because the ISD products are top quality we wanted to follow their recommended audio design practices:

- analog components are placed physically close to the IC with short leads
- analog and digital power & ground tracks have been kept separate
- large power & ground tracks have been used as much as possible even between IC pads

R1 & R8 are just able to squeeze in between the sides of the IC socket. The 1uF mini electrolytic capacitor C7 will fold over next to R11 quite comfortably. **NOTE:** there is one link to make under the socket. Use some wire cut off from a resistor to make the link.

Operation

When you first use the Recorder attach a speaker (4 ohm or 8 ohm) to the Output and record & play-back your messages as previously described.

If you want more loudness ISD suggest that one way to do so is to limit the low end frequency response. With C4 & C6 at 0.1uF, signals above 160Hz are not attenuated. Changing these capacitors to 0.01uF increases this low end pole to 1500Hz. Since small speakers do not reproduce the low frequencies efficiently this change may give you an increase in loudness.

If you want to amplify the output the differential output may be fed directly to audio equipment with a differential input. Or you may use an amplifier like an LM386. If you use the amplifier between one output pin (either pin 14 or 15) and ground it is very important that the unused output pin not be grounded. It must be left unconnected.

If It Does Not Work. Check that the diodes are all in the correct way. Are the resistors in the right places. Check that the TO-92 packaged components are in their correct places. Are the capacitors, microphone & LEDs the correct way around.

More on the ISD25xxx

The power of the chip lies in the fact that the memory space is computer addressable. In the ISD25xx there are 600 (six hundred) addressable message segments. So in the ISD2560, for example, you can record a maximum of 600 messages each 100 msec long. So who wants 600 1/100th second messages? Well think of a talking voltmeter. No more would you have to put the probes on then move your head & eyes to read the display. The meter would say "six point two five volts". The spoken numerals plus the teens, tens & other quantifiers would only occupy the exact memory space they need to the next 1/100th of a second. The micro-controllers job is to quickly search through the address space and put together the required message output in real time.

CK1213 - 40 Second Message Recorder with Looping Option

Think of a burglar alarm system: both the setting of it and the spoken messages it could give (over the phone after using the DTMF tones of phone numbers stored in ISD25xx memory too) after it was set off. Think of setting a VCR: instruction about how to set it can be spoken to you. And there would even be space for 'Have a nice day' at the end of it.

Also ISD25xx chips can (with one exception) be seamlessly connected together to give increased message time. By seamless is meant that a message can straddle 2 physical IC's. (Earlier ISD chips could not do this.) See the Data Sheet for more information.

All ISD chips in the 25xxx series can be used in this kit. They all Loop when pin 4 is taken HI. We provide the ISD2540, 40 second chip here. We provide the ISD25120, 120 second chip with Kit 64.

See our website at <http://www.electronickits.com>

COMPONENTS

Resistors:

680R blue grey brown R5 R6	2
1K brown black red R7	1
4K7 yellow violet red R2	1
10K brown black orange R8 R9	2
22K red red orange R3 R4	2
100K brown black yellow R10 R11	2
470K yellow violet yellow R1	1

Capacitors:

0.1 Monoblock 104 C1 C2 C4 C6	4
1uF electrolytic mini C7	1
4.7uF elcap C8	1
100uF elcap C3	1
220uF elcap C5	1
BC547 Q1 Q2	2
BC557 Q3	1
ISD2540 IC	1
28 pin IC socket	1
1N4148 diode	1
2 pole terminal block	2
Electret Microphone	1
Hat keyswitch	2
5mm LED	2
K146 PCB	1
SPDT PCB mounted switch	2

